

# Three-phase systems in sinusoidal steady state, per-unit analysis

ELEC0447 - Analysis of electric power and energy systems

Bertrand Cornélusse

September 5, 2025

# Overview

1. Three-phase systems (reminder)
2. Neutral break exercise
3. Per-phase analysis
4. Power transfer between AC systems
5. Per-unit normalization

# What will we learn today?

Mostly from Chapter 2 of Ned Mohan's book:


Mohan, Ned. Electric power systems: a first course. John Wiley & Sons, 2012.

- ▶ 3-phase systems
- ▶ Power transfer between AC systems
- ▶ Per unit normalization

You will be able to do exercises 2.1, 2.2, 2.4, 2.5, 2.9, 2.11, 2.12, 2.14, 2.16, 2.17, 2.18, 2.19 and 2.20 from the Ned Mohan's book.

## Three-phase systems (reminder)

# Three-phase system

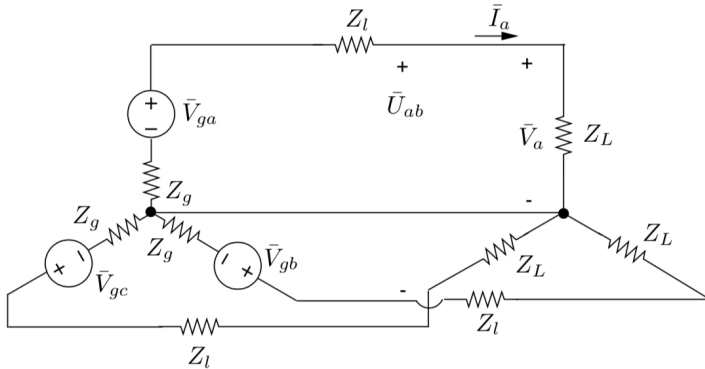

**Figure 1:** Generation -> transmission -> load


Here the load is connected as a *star*. A neutral point is present. The neutral conductor is not necessarily implemented.

By design the voltage sources are shifted by  $120^\circ$


$$\bar{V}_{ga} = V e^{j\phi_u}$$

$$\bar{V}_{gb} = V e^{j(\phi_u - 2\pi/3)} = \bar{V}_{ga} e^{-j2\pi/3}$$
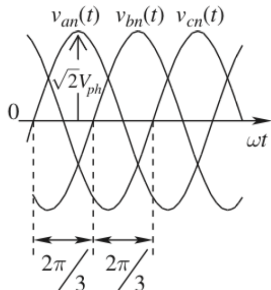
$$\bar{V}_{gc} = V e^{j(\phi_u - 4\pi/3)} = \bar{V}_{ga} e^{-j4\pi/3}$$



(a)

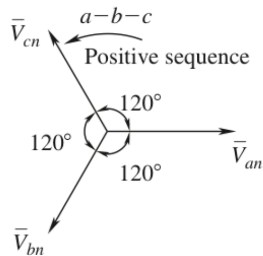

(b)


Three-phase voltages in time and phasor domain.

# Phase voltage vs. line to line voltage

These voltages represent the **phase voltages**. If we now look at the **line to line voltages**:

$$\bar{U}_{ab} = \bar{V}_{ga} - \bar{V}_{gb} = \sqrt{3}\bar{V}_{ga}e^{j\pi/6}$$

and similarly for  $\bar{U}_{bc}$  and  $\bar{U}_{ca}$ .

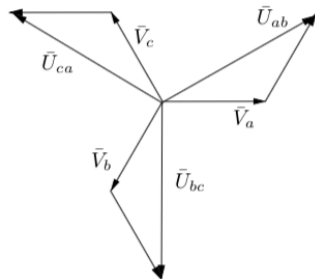

**Figure 2:** Line vs. phase voltages

*Example:* My house is fed by a 400V three-phase system. This means the line voltages are 400V (rms), and thus phase voltages are 230V (approximately). Typically, the phase voltages are distributed independently in the house, each with the neutral.

# Total power

The total complex power transmitted to the load is

$$S = \sum_{k \in \{a,b,c\}} \bar{V}_{gk} \bar{I}_k^*$$

Hence in a balanced system the total active power to the load is  $3VI \cos \phi$ , with 3 or 4 wires (instead of 2 in a single-phase system).



# Comments

- ▶ In every phase there is a current flowing. In a balanced system, currents are phase shifted by  $120^\circ$  and sum to zero. Thus the neutral can in theory be removed. This is done in some portions of the global system (typically at high voltage), where neutral points are grounded.
- ▶ Some loads can also be connected in "delta", hence the neutral is not accessible.
- ▶ Finally, in unbalanced systems, currents are dictated by the impedances seen in the different phases. There is no perfectly known relation, a priori.

Neutral break exercise

# Neutral break: problem statement

Consider a 3-phase Y-connected resistive circuit with unbalanced resistors in the phases. In normal operation there is a neutral wire. Then the neutral breaks.

- ▶ Compute in both cases the voltages across the resistors, the currents and the consumed powers.
- ▶ What can you observe?

**Remark:** In the next slides, the phasor notation is omitted, but all voltages and currents should be understood as phasors.

# Case 1: Neutral Connected

## Assumptions:

- ▶ 3-phase balanced voltage supply:  $V_{ab} = V_{bc} = V_{ca} = V_L$  (line-to-line voltage)
- ▶ Phase voltages (line-to-neutral) are given by  $V_{an} = V_{bn} = V_{cn} = \frac{V_L}{\sqrt{3}}$ , and the angle between them is  $120^\circ$ .
- ▶ Unbalanced resistances:  $R_a, R_b, R_c$  (different resistances in each phase).

# Voltages and currents

**Voltages:** In normal operation, with the neutral connected, each resistor has its corresponding phase voltage across it:

$$V_{R_a} = V_{an}, \quad V_{R_b} = V_{bn}, \quad V_{R_c} = V_{cn}$$

**Currents:** The current in each phase is given by Ohm's law:

$$I_a = \frac{V_{an}}{R_a}, \quad I_b = \frac{V_{bn}}{R_b}, \quad I_c = \frac{V_{cn}}{R_c}$$

The neutral current,  $I_n$ , is the sum of the phase currents:

$$I_n = I_a + I_b + I_c$$

Due to the unbalanced resistances,  $I_n$  will not be zero.

# Powers

The power consumed in each phase is:

$$P_a = V_{an}I_a = \frac{V_{an}^2}{R_a}, \quad P_b = \frac{V_{bn}^2}{R_b}, \quad P_c = \frac{V_{cn}^2}{R_c}$$

Total power consumed:

$$P_{\text{total}} = P_a + P_b + P_c$$

## Case 2: Neutral Broken

When the neutral breaks, the three resistors form a system without a direct connection to the neutral point. The current through each resistor still needs to sum to zero because the current has no return path through the neutral. This changes the voltage distribution across the resistors.

# Voltages and currents

Here,  $V_{nN'}$  is an unknown voltage offset at the floating point  $N'$  (the shifted neutral). Using KCL, you solve for this voltage by ensuring the sum of the currents at  $N'$  is zero:

$$\frac{V_{aN'}}{R_a} + \frac{V_{bN'}}{R_b} + \frac{V_{cN'}}{R_c} = 0$$

Solving this system gives you the new voltages across the resistors.

- The currents in each phase are then given by:

$$I_a = \frac{V_{aN'}}{R_a}, \quad I_b = \frac{V_{bN'}}{R_b}, \quad I_c = \frac{V_{cN'}}{R_c}$$

- Since the neutral is broken, the sum of these currents must equal zero:

$$I_a + I_b + I_c = 0$$



# Powers

- The power consumed in each phase is:

$$P_a = V_{aN'} I_a = \frac{(V_{aN'})^2}{R_a}, \quad P_b = \frac{(V_{bN'})^2}{R_b}, \quad P_c = \frac{(V_{cN'})^2}{R_c}$$

- Total power consumed:


$$P_{\text{total}} = P_a + P_b + P_c$$

# Observations

- ▶ When the neutral is connected, the voltages across the resistors are straightforwardly determined by the phase-to-neutral voltages.
- ▶ When the neutral is broken, the voltage distribution becomes more complex, and the voltages across the resistors are no longer the same as the phase-to-neutral voltages. The total current in the system remains zero, and the power distribution can also change depending on the values of the resistors.

A numerical example here.
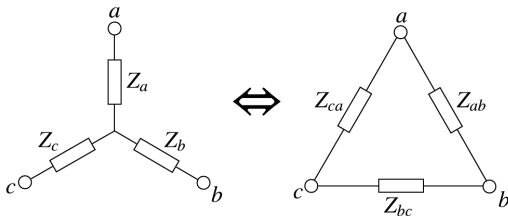
## Useful formulas: from star to delta connection (and back)



$$Z_a = \frac{Z_{ab}Z_{ca}}{Z_{ab} + Z_{bc} + Z_{ca}}$$

$$Z_b = \frac{Z_{bc}Z_{ab}}{Z_{ab} + Z_{bc} + Z_{ca}}$$

$$Z_c = \frac{Z_{ca}Z_{bc}}{Z_{ab} + Z_{bc} + Z_{ca}}$$


$$Z_{ab} = \frac{Z_aZ_b + Z_bZ_c + Z_cZ_a}{Z_c}$$

$$Z_{bc} = \frac{Z_aZ_b + Z_bZ_c + Z_cZ_a}{Z_a}$$

$$Z_{ca} = \frac{Z_aZ_b + Z_bZ_c + Z_cZ_a}{Z_b}$$

What happens in a balanced system?


# Per-phase analysis

The background of the slide features a white upper half and a teal lower half. The teal section is composed of two large triangular shapes that meet at a central point at the bottom, creating a V-shape. The teal color is a dark, muted blue-green.
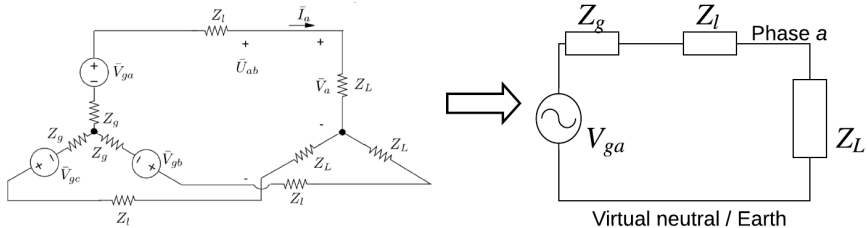
# Per-phase analysis I

In a **balanced** system, analyses can be simplified by representing only one phase.

This is straightforward if there are no couplings between phases.



## Per-phase analysis II

In case there is a coupling, and that for instance the voltage drop  $\bar{V}_{aA}$  along a line presenting an impedance  $Z_{self}$  traversed by a current  $\bar{I}_a$  is also function of the currents in the other phases:


$$\bar{V}_{aA} = Z_{self}\bar{I}_a + Z_{mutual}\bar{I}_b + Z_{mutual}\bar{I}_c$$

then the per-phase equivalent impedance (for phase  $a$ ) is

$$Z_{aA} = Z_{self} - Z_{mutual}$$

since  $\bar{I}_a + \bar{I}_b + \bar{I}_c = 0$

# One-line diagram

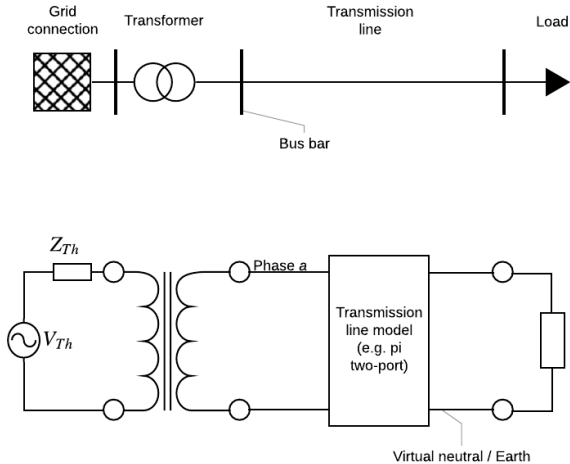

# Power transfer between AC systems


The background of the slide features a white central area where the text is located. This central area is framed by two large teal-colored triangles that point towards each other from the left and right sides, meeting at a point at the bottom center. The overall effect is a stylized, modern graphic design.


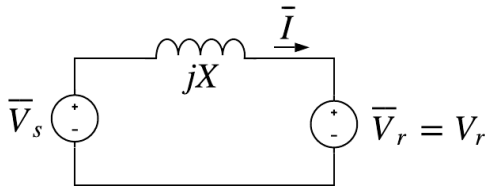
# Power transfer between AC systems I

Consider the following simple system. We

have  $\bar{I} = \frac{\bar{V}_s - \bar{V}_r}{jX}$



Let  $\delta$  be the angle between  $\bar{V}_r$  and  $\bar{V}_s$ , then

$$\begin{aligned} S_r &= \bar{V}_r \bar{I}^* = V_r \left( \frac{V_s \angle -\delta - V_r}{-jX} \right) \\ &= \frac{V_s V_r \sin \delta}{X} + j \frac{V_s V_r \cos \delta - V_r^2}{X} \end{aligned}$$

# Power transfer between AC systems II

Let's remember two things:

- ▶ The **active** power is highly sensitive to  $\delta$
- ▶ The **reactive** power acts on the **voltage magnitude** (look at what happens for  $\delta = 0$ )

See [a demo](#).

# Per-unit normalization

The background of the slide features a white central area where the text is located. This central area is framed by two large teal-colored triangles that point towards each other from the left and right sides, meeting at a point at the bottom center. The overall effect is a stylized, modern graphic design.

# Per-unit values

Per-unit values are the ratio between the actual value and the base value.

$$\text{Value}_{pu} = \frac{\text{Actual value}}{\text{Base value}}$$

It is useful in electrical power systems for two reasons:

- ▶ The parameters of rotating machines and transformers provided by the manufacturers are often given in pu.
- ▶ In a transformer, the impedance (in ohm) changes according to the square of the voltage ratio. If we express the impedance in pu, the value is invariant from one side of the transformer to the other.

In an electric network, a single base power is sufficient for the whole system, but for a system with transformers, one base voltage per voltage level is preferable.

## Example I

It is **known** that the internal reactance of a synchronous machine lies typically in the range  $[1.5, 2.5]$  pu (on the machine base)!

A machine with the characteristics (20 kV, 300 MVA) has a reactance of  $2.667 \Omega$ .

Is this a normal value?

- ▶ (Here we do not need a base value for time)
- ▶ The base impedance is  $Z_B = 20^2/300 = 1.333 \Omega$
- ▶ Hence the value of the reactance in per unit is  $2.667/1.333 = 2 \text{ pu}$
- ▶ This is a quite normal value!

## Example II

Same question for a machine with the characteristics (15 kV, 30 MVA)

- ▶ The base impedance is now  $Z_B = 15^2/30 = 7.5 \Omega$
- ▶ The value of the reactance in per unit is  $2.667/7.5 = 0.356 pu$
- ▶ Hence an abnormal small value!

## Per unit in three-phase systems

Let the base power  $S_B$  be the three-phase power, and  $U_b = \sqrt{3}V_B$  be the line to line voltage base.

The (single-phase) base current is

$$I_B = \frac{S_B}{3V_B} = \frac{S_B}{\sqrt{3}U_B}$$

The base impedance is

$$Z_B = \frac{V_B}{I_B} = \frac{3V_B^2}{S_B} = \frac{U_B^2}{S_B}$$

In a single phase equivalent representation, the power values in per unit can be multiplied by  $S_b$  to get the total three-phase power.