

# **ELEC0447 – Analysis of electric power and energy systems**

Sinusoidal steady-state analysis

Bertrand Cornélusse  
[bertrand.cornelusse@uliege.be](mailto:bertrand.cornelusse@uliege.be)

# What will we learn today?

- Recap of conventions
- Sinusoidal steady state analysis

You will be able to do exercises 2.1, 2.2, 2.4, 2.5, 2.9, 2.11, 2.12, 2.14, 2.16, 2.17, 2.18, 2.19 and 2.20 from the Ned Mohan's book.

# Basics and conventions

## Power and energy

- Power measures the rate of use of energy
- It is expressed in Watt [W]: 1 W = 1 Joule/second
- In an electric system,

$$p(t) = u(t) \times i(t)$$

- $u(t)$  is the voltage measured in volt [V], the line integral of the electric field between two points.
  - $i(t)$  is the current measured in amps [A]
  - $t$  is the time
- To measure energy in power systems, we use units ranging from a kWh (a microgrid) to a TWh (a country)
- Devices have power ratings ranging from W to GW (although we generally speak in VA for ratings)




Olympic Cyclist Vs. Toaster: Can He Power I...



Watch Later




Share

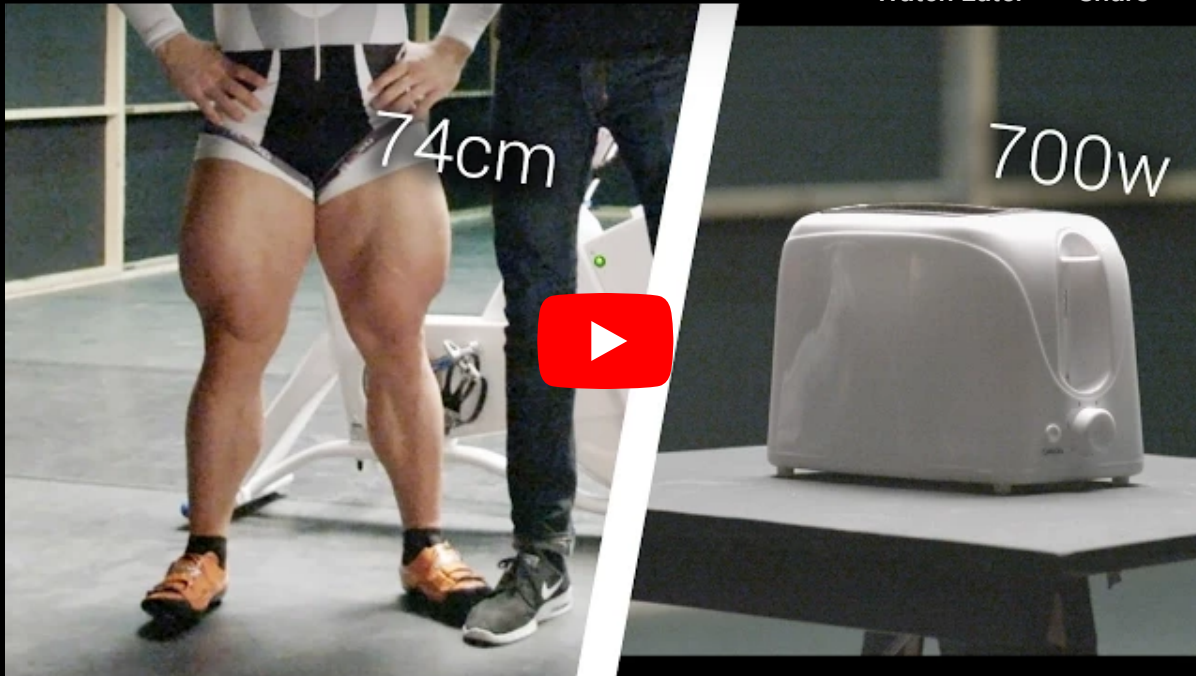

The cyclist vs the toaster.
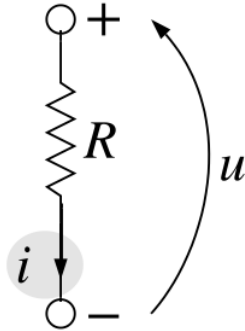
## Motor convention (or standard reference)

When using the motor convention to direct  $u$  w.r.t.  $i$ ,  $p(t)$  represents the power **consumed** by a device (here a resistor):



- The power consumed can be  $< 0$ ,  $= 0$ , or  $> 0$  depending on the device
- E.g. for a resistor we always have  $p(t) \geq 0$
- The **opposite** convention is the **generator convention**
- We will sometimes use a mix of both conventions, based on intuition, so that in general we have few negative numbers: pay attention to the orientations!

## Magnetic fields, etc.

Magnetic fields have a central role to model the behavior of equipment (lines, transformers, generators, etc.).

As this course will not be focused on modeling devices, but rather a system of devices, magnetic effects will often be highly abstracted (an inductance, or a turns ratio).

Let's just recall that

- a magnetic field is due to charges in movement or magnetized materials
- it is measured in amps/meter (for  $H$ ) or in Tesla (for  $B$ ) when we capture the effect of the material (the  $\mu_0$  coefficient in the air)
- the magnetic flux ( $\phi$  in weber) measures the magnetic field crossing a surface
- a time varying magnetic flux induces a voltage (Lenz), this is the fundamental principle behind transformers.

# **Sinusoidal steady state analysis**



## Sinusoidal signals and phasor representation

Unless otherwise specified, we will always work with sinusoidal signals and in steady state:

$$y(t) = \sqrt{2}Y \cos(\omega t + \phi_y).$$


$Y$  is the **rms** value of the signal,  $\phi_y$  its phase and  $\omega$  its angular frequency.

At a specific frequency  $f = \frac{\omega}{2\pi}$ , the signal can be represented as a phasor

$$\bar{Y} = Y \angle \phi_y = Y e^{j\phi_y}$$

Phasors allow to work in the frequency domain, which is much more handy for computations.

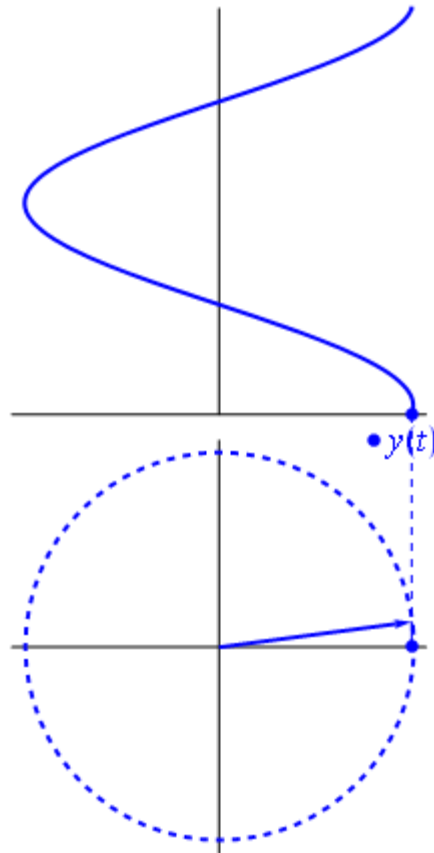How do you get the time expression from the phasor?



<https://en.wikipedia.org/wiki/Phasor>

# Impedance

Let  $u(t)$  and  $i(t)$  be the voltage and current across a one-port, respectively, in sinusoidal steady state and with the motor convention.

- For a resistor,  $u(t) = Ri(t)$  hence  $\bar{U} = R\bar{I}$
- For a self,  $u(t) = L\frac{di(t)}{dt}$  hence  $\bar{U} = j\omega L\bar{I}$
- For a capacitor,  $i(t) = C\frac{du(t)}{dt}$  hence  $\bar{I} = j\omega C\bar{U}$

The **impedance**, a complex number, generalizes this notion

$$Z = R + jX \quad [\Omega]$$

such that  $\bar{U} = Z\bar{I}$  with

- for a resistor,  $Z = R$
- for a self,  $Z = jX = j\omega L$
- for a capacitor,  $Z = jX = -j\frac{1}{\omega C}$

## Impedance, admittance, etc.

The imaginary part of the impedance,  $X$ , is called reactance

The admittance  $Y$  is the inverse of the impedance, expressed in Siemens:

$$Y = G + jB$$

- $G$  is the conductance
- $B$  is the susceptance




## AC current impedance - Alternating Voltage ...



Watch Later



Share

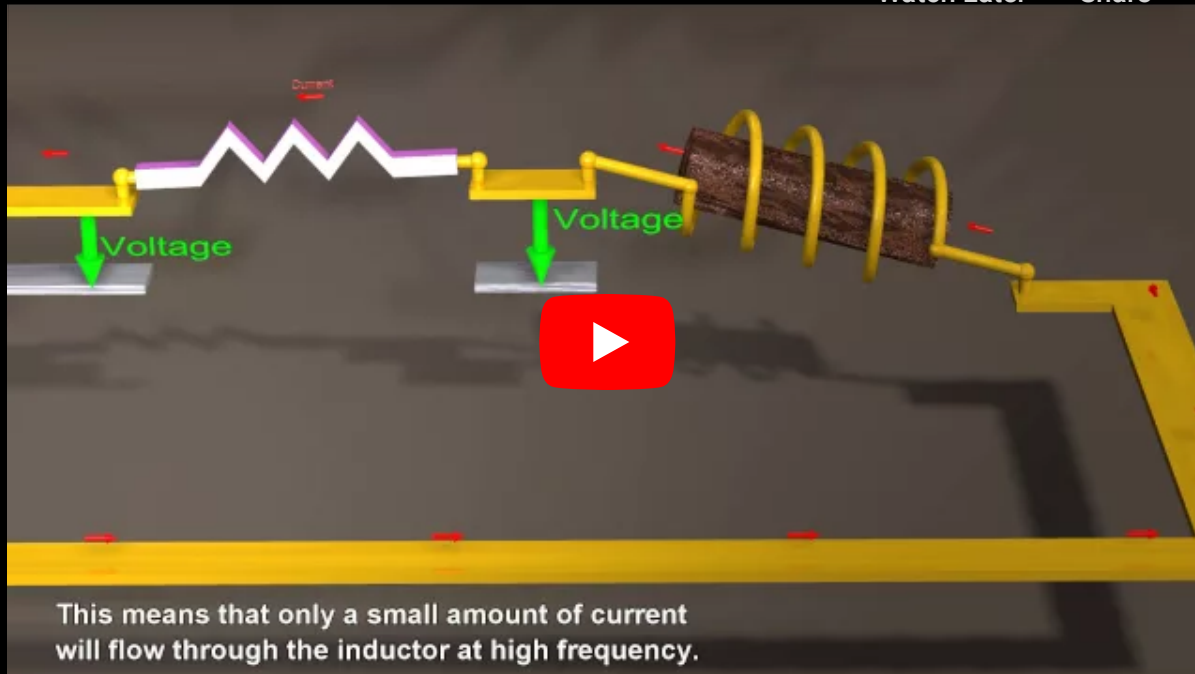

A nice animation.

## Complex calculus


$$|Z| = \sqrt{R^2 + X^2}$$

$$\angle Z = \arctan \frac{X}{R}$$



$$Z = \frac{\bar{U}}{\bar{I}} = \frac{U}{I} \angle (\phi_u - \phi_i)$$

# Phasor diagrams

Plot the phasors in the complex plane!

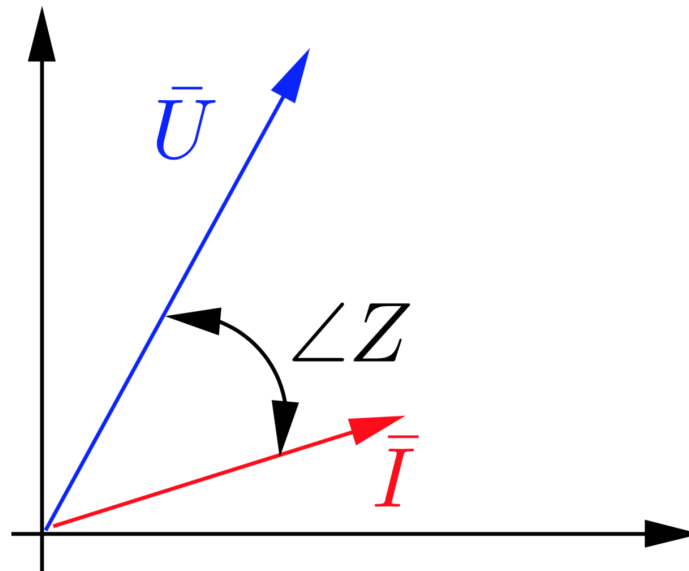

Inductive or capacitive? Which is which?

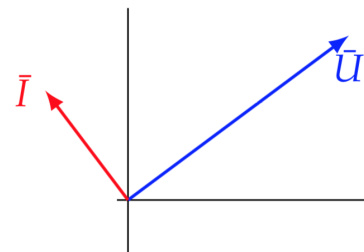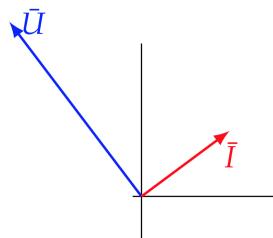

## The notions of power

The complex power is defined as

$$S = \bar{U} \bar{I}^*$$

Let

$$\phi = \phi_u - \phi_i$$

then

$$S = UIe^{j\phi} = P + jQ$$

- $P = UI \cos \phi$  is the active power, measured in watt
- $Q = UI \sin \phi$  is the reactive power, measured in var
- $\cos \phi$  is the power factor

Reactive power is, in general, undesirable.

The apparent power is  $|S| = UI$ , measured in VA



## Useful formulas - leading and lagging circuits

$$P = RI^2 = \frac{U^2}{R}$$

$$Q = XI^2 = \frac{U^2}{X}$$


$$\tan \phi = \frac{Q}{P}$$

$$\cos \phi = \frac{P}{|S|}$$

The power factor does not tell you whether the system is **leading** or **lagging**

- in an inductive system,  $u(t)$  precedes  $i(t)$ ,  $i(t)$  is **lagging**, thus  $Q > 0$  (motor convention)
- in a **capacitive** system, this is the opposite (**leading**).

## Power factor compensation

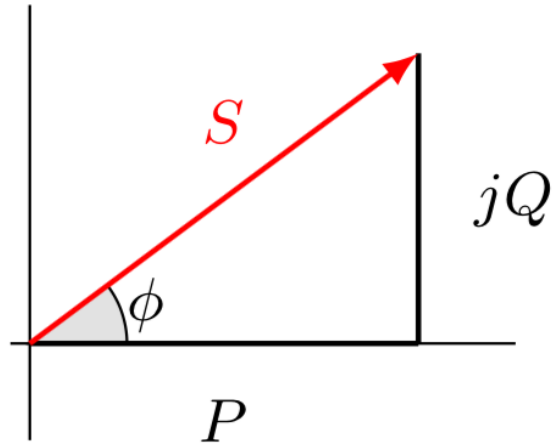

Produce some  $Q$  to cancel out  $\phi$ .

Example:

A 120V voltage source at 60 Hz that feeds a R-L load  $1858.4 + j1031.4 \text{ VA}$

